


Project Title:

CMOS digital phase frequency detector.


Design Goals:

- *To design a phase and frequency detector for two different signals.*
- *To determine whether there is any phase or frequency error in between input and output signals.*
- *Therefore, by detecting the error we came to know what is the change that the circuit **or** channel where the input signal is given was altering the phase or frequency of input signal.*

Block diagram of design:

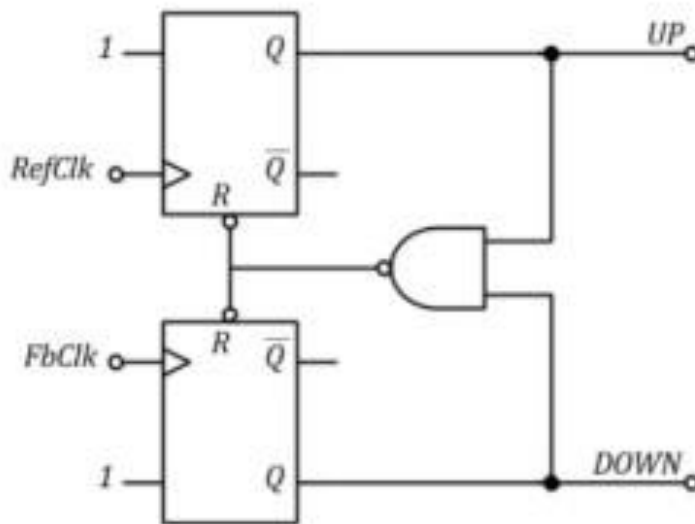

Schematic Diagram:

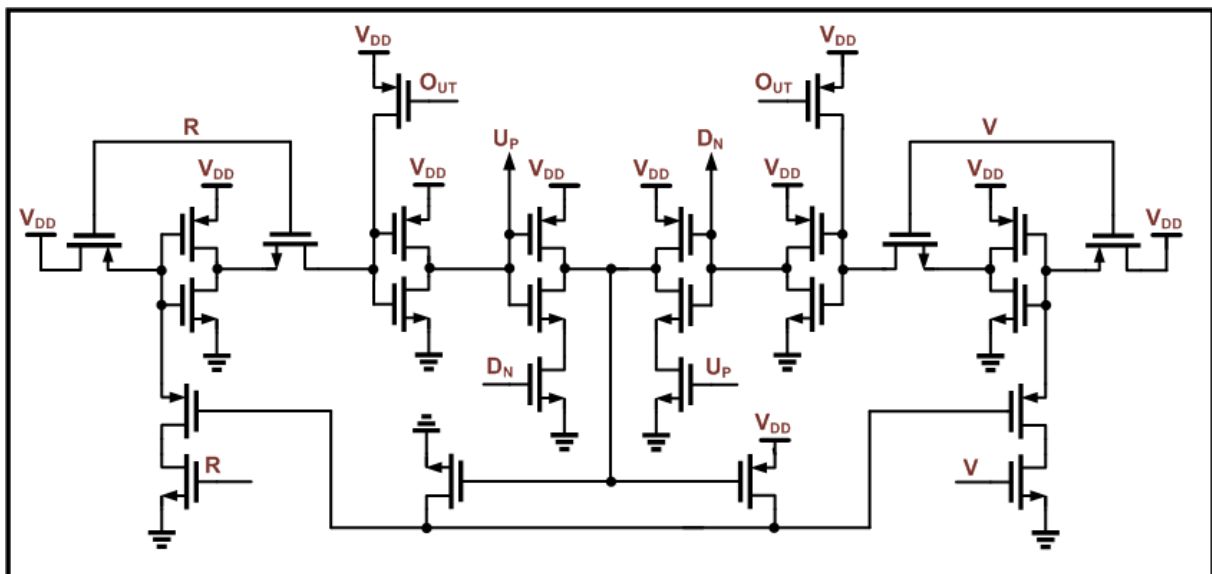

References:

1. https://en.wikipedia.org/wiki/Phase_detector#References
2. <https://analog.intgckts.com/phase-locked-loop/phase-frequency-detector/>
3. Electronic Circuits: Linear/Analog Louis E. Frenzel Jr., in Electronics Explained (Second Edition), 2018.
4. CMOS phase frequency detector for high-speed applications.
<https://ieeexplore.ieee.org/document/5418651>

Team members:

K.Ramamohan Reddy. (mentor)

Mangalapally Naveen Kumar.

Bommakanti Pravali.